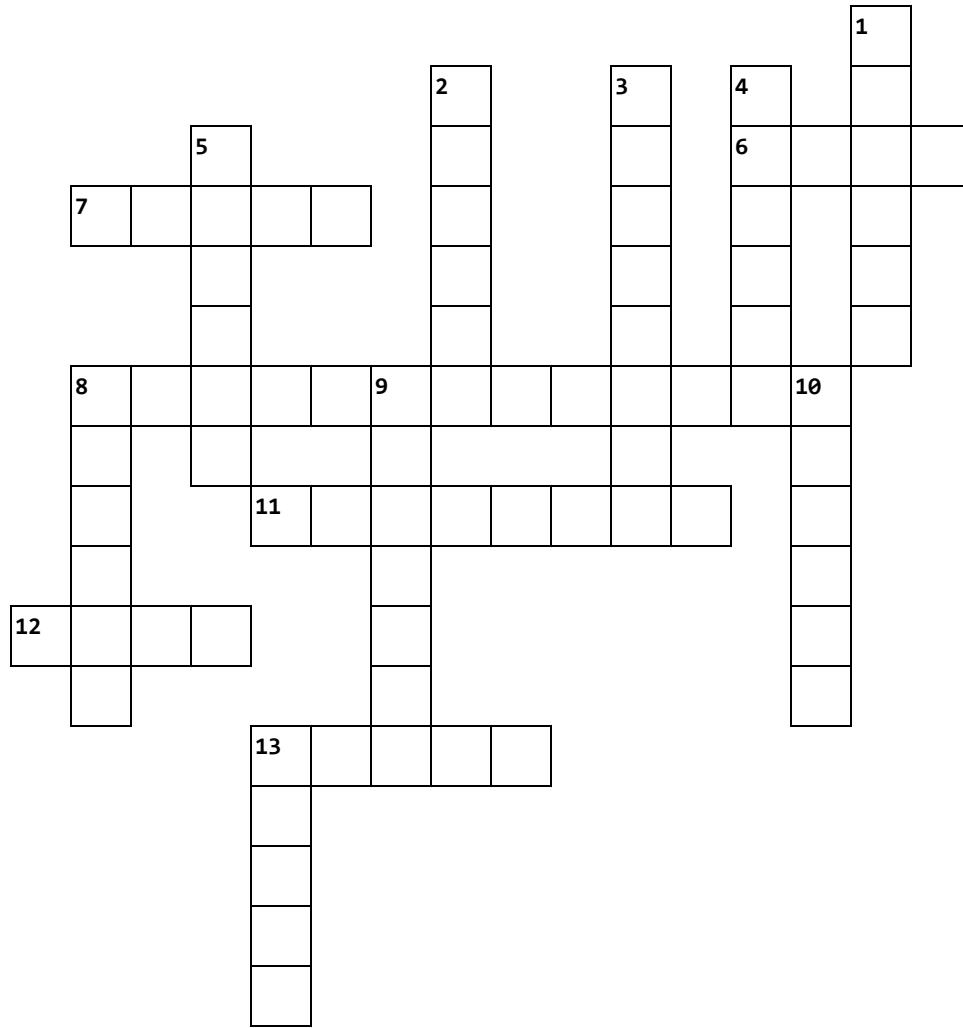


Series and Parallel Circuits pg. 15-20



Across

- 6. An incomplete circuit is also called this.
- 7. The energy in the D-cell will do this much faster in a parallel circuit.
- 8. These are the places where the wires touch the components.
- 11. In this circuit each component has its own pathway.
- 12. A battery is also called this.
- 13. This is an example of a component.

Down

- 1. Electric current comes from this type of source.
- 2. If you want these types of light, put the lightbulbs in this.
- 3. One end of a battery cell is call positive. The other one is called this.
- 4. An energy source might be one of these.
- 5. The metal part of the lightbulb is called this.
- 8. If a circuit is complete, it is also called this.
- 9. The pathway through which the electric current flows is called this.
- 10. If the current flows through two lightbulbs in one circuit it is called this.
- 13. These types of wires carry electricity.